

Question

An electric iron consumes energy at a rate of 880 W when heated. If the source voltage is 220 V, calculate the current and resistance.